 


# BITBOT Architecture


CSCE 312: Computer Organization



# Overview

- While HACK is a great introduction to assembly language, it does not reflect popular assembly languages used in 2023
- Introducing BITBOT, a simplified RISC CPU architecture modelled heavily after MIPS/ARM
- BITBOT computer contains 3 parts:
  - ROM32K
  - CPU
  - Data Memory

# Overview

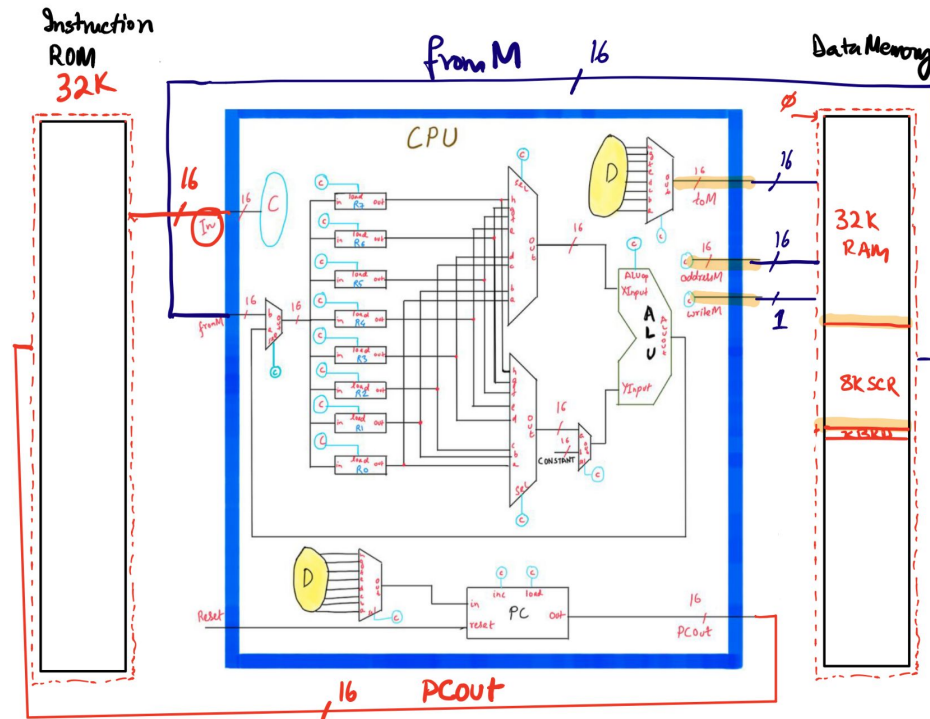

# ROM32K


- BUILT-IN chip
- No need to do anything beside connecting it to the computer

# CPU

- Extension of TOY CPU to support a wider range of instructions
- 16-bit architecture (i.e. a word is defined as 16 bits)
- 8 General Purpose Registers, 16-bit
 
# Data Memory

- 40K+1 16-bit data words
- Divided into 3 regions
  - 32K words for holding data (RAM)
  - 8K words for memory-mapped screen output
  - 1 word for memory-mapped keyboard input device



# Computer

- Combine 3 parts together
- Only for wiring parts, no additional logic required

# Further details

- The recommended order of implementation:
  - Data Memory
  - CPU
  - Computer



# Further details: Memory

- Built-in chips: RAM32K(in=, load=, address=, out=), Screen(in=, load=, address=, out= ), Keyboard(out= )
  - RAM32K: only bit 14 to 0 are used ( $2^{15} = 32K$ ), thus must check address[15] = 0 and load = 1 before accessing the RAM
  - Screen: use address[13..15] for loading (load if it is 100), address[0..12] is for the mapped memory positions on the screen
  - Keyboard: should be self-explanatory
  - Use a Mux8Way16 to glue everything together, use the hint above to figure out the correct selector bits


# Further details: CPU

- Schematic mostly given for datapath
- Recommended strategy for controlpath:
  - Go through each instruction (start with a set of instructions)
  - Register control (whenever register is written to)
  - Arithmetic (ALU)
  - Memory read/write (addressM, writeM, toM, and Screen)
  - Branching (control the PC)

# Further details: CPU – example

- Let's look at designing the controlpath for register control

# Further details: CPU – example

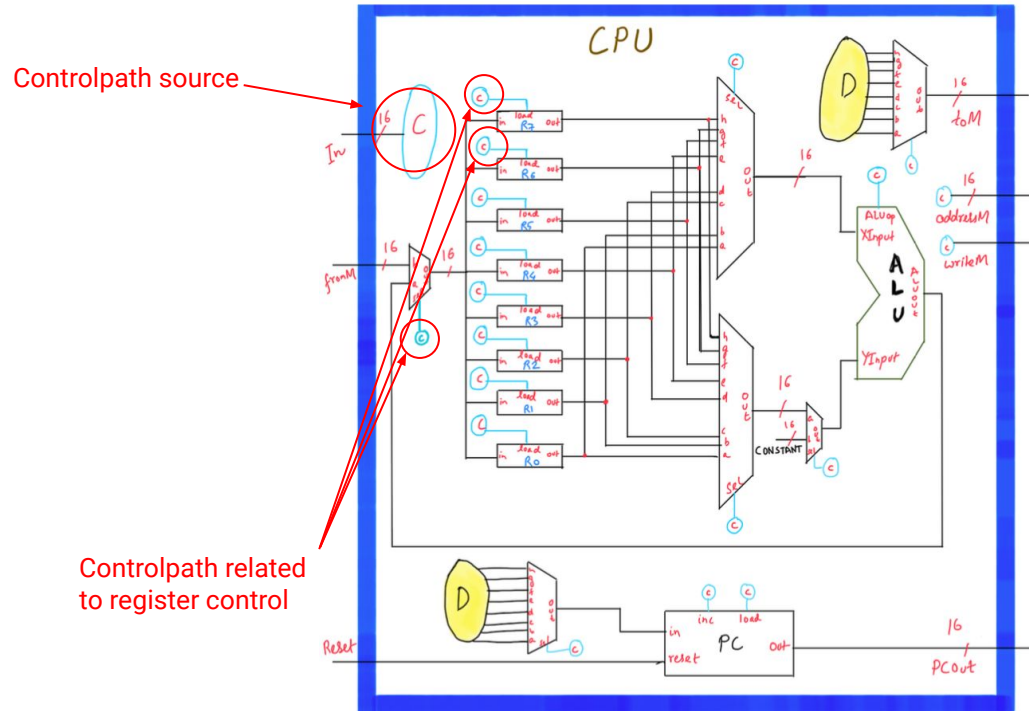

# Further details: CPU – example

Arithmetic	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		DEST REGISTER			SRC1 REGISTER			SRC2 REGISTER					
ADD	ADD R0, R1, R2 (i.e. R0 = R1 + R2)	0	0	0	0	Any Reg: 000 to 111			Any Reg: 000 to 111			Any Reg: 000-111					
ADDI	ADDI R0, R1, 8 (i.e. R0 = R1 + 8)			0	1							Six Bit Immediate Value (0-63)					
SUB	SUB R0, R1, R2 (i.e. R0 = R1 - R2)			1	0							Any Reg: 000-111					
SUBI	SUBI R0, R1, 8 (i.e. R0 = R1 - 8)			1	1							Six Bit Immediate Value (0-63)					
Logical	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		DEST REGISTER			SRC1 REGISTER			SRC2 REGISTER			UNUSED		
NAND	NAND R0, R1, R2 (i.e. R0 = R1 NAND R2)	0	1	0		Any Reg: 000 to 111			Any Reg: 000 to 111			Any Reg: 000 to 111					
NOR	NOR R0, R1, R2 (i.e. R0 = R1 NOR R2)			1													
Memory	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		LEFT SIDE			RIGHT SIDE								
READ	READ R0, R1 (i.e. R0 = MEM[R1])	1	0	0	0	DEST REGISTER			SRC PTR REGISTER								
WRITE	WRITE R0, R1 (i.e. MEM[R0] = R1)			1	0	DEST PTR REGISTER			SRC REGISTER								
Branch	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		TARGET ADDRESS			SRC REGISTER								
JMP	JMP R0 (i.e. PCOut = R0)	1	0	1	1	Any Reg: 000 to 111											
BEQ	BEQ R0, R1 (i.e. PCOut = R0 if R1==0)			0	1				Any Reg: 000 to 111								
INPUT/OUTPUT	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		TARGET ADDRESS			SRC REGISTER								
INP	INP R0 (i.e. R0 = MEM[KEYBOARD])	1	1	1	0	Any Reg: 000 to 111											
OUT	OUT R0, R1 (i.e. SCREEN[R0] = R1)			0	0				Any Reg: 000 to 111								

## Further details: CPU – example

Arithmetic	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		DEST REGISTER			SRC1 REGISTER			SRC2 REGISTER					
ADD	ADD R0, R1, R2 (i.e. R0 = R1 + R2)	0	0	0	0	Any Reg: 000 to 111			Any Reg: 000 to 111			Any Reg: 000-111					
ADDI	ADDI R0, R1, 8 (i.e. R0 = R1 + 8)			0	1							Six Bit Immediate Value (0-63)					
SUB	SUB R0, R1, R2 (i.e. R0 = R1 - R2)			1	0							Any Reg: 000-111					
SUBI	SUBI R0, R1, 8 (i.e. R0 = R1 - 8)			1	1							Six Bit Immediate Value (0-63)					
Logical	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		DEST REGISTER			SRC1 REGISTER			SRC2 REGISTER			UNUSED		
NAND	NAND R0, R1, R2 (i.e. R0 = R1 NAND R2)	0	1	0		Any Reg: 000 to 111			Any Reg: 000 to 111			Any Reg: 000 to 111					
NOR	NOR R0, R1, R2 (i.e. R0 = R1 NAND R2)			1													
Memory	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		LEFT SIDE			RIGHT SIDE								
READ	READ R0, R1 (i.e. R0 = MEM[R1])	1	0	0	0	DEST REGISTER			SRC PTR REGISTER								
WRITE	WRITE R0, R1 (i.e. MEM[R0] = R1)			1	0	DEST PTR REGISTER			SRC REGISTER								
Branch	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		TARGET ADDRESS			SRC REGISTER								
JMP	JMP R0 (i.e. PCOut = R0)	1	0	1	1	Any Reg: 000 to 111											
BEQ	BEQ R0, R1 (i.e. PCOut = R0 if R1==0)			0	1												
INPUT/OUTPUT	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		TARGET ADDRESS			SRC REGISTER								
INP	INP R0 (i.e. R0 = MEM[KEYBOARD])	1	1	1	0	Any Reg: 000 to 111											
OUT	OUT R0, R1 (i.e. SCREEN[R0] = R1)			0	0												

# Further details: CPU – example

Arithmetic	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		DEST REGISTER			SRC1 REGISTER			SRC2 REGISTER					
ADD	ADD R0, R1, R2 (i.e. R0 = R1 + R2)	0	0	0	0	Any Reg: 000 to 111			Any Reg: 000 to 111			Any Reg: 000-111					
ADDI	ADDI R0, R1, 8 (i.e. R0 = R1 + 8)			0	1							Six Bit Immediate Value (0-63)					
SUB	SUB R0, R1, R2 (i.e. R0 = R1 - R2)			1	0							Any Reg: 000-111					
SUBI	SUBI R0, R1, 8 (i.e. R0 = R1 - 8)			1	1							Six Bit Immediate Value (0-63)					
Logical	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		DEST REGISTER			SRC1 REGISTER			SRC2 REGISTER			UNUSED		
NAND	NAND R0, R1, R2 (i.e. R0 = R1 NAND R2)	0	1	0		Any Reg: 000 to 111			Any Reg: 000 to 111			Any Reg: 000 to 111					
NOR	NOR R0, R1, R2 (i.e. R0 = R1 NAND R2)			1													
Memory	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		LEFT SIDE			RIGHT SIDE								
READ	READ R0, R1 (i.e. R0 = MEM[R1])	1	0	0	0	DEST REGISTER			SRC PTR REGISTER								
WRITE	WRITE R0, R1 (i.e. MEM[R0] = R1)			1	0	DEST PTR REGISTER			SRC REGISTER								
Branch	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		TARGET ADDRESS			SRC REGISTER								
JMP	JMP R0 (i.e. PCOut = R0)	1	0	1	1	Any Reg: 000 to 111											
BEQ	BEQ R0, R1 (i.e. PCOut = R0 if R1==0)			0	1				Any Reg: 000 to 111								
INPUT/OUTPUT	EXAMPLE	In[15]	In[14]	In[13]	In[12]	In[11]	In[10]	In[9]	In[8]	In[7]	In[6]	In[5]	In[4]	In[3]	In[2]	In[1]	In[0]
		OPCODE		OPTYPE		TARGET ADDRESS			SRC REGISTER								
INP	INP R0 (i.e. R0 = MEM[KEYBOARD])	1	1	1	0	Any Reg: 000 to 111											
OUT	OUT R0, R1 (i.e. SCREEN[R0] = R1)			0	0				Any Reg: 000 to 111								

# Further details: CPU

When design controlpath, ALWAYS look at the register sheet



# Further details: Computer

- Instantiate the ROM32K
- That's it :)

# Where to find additional information

- Provided resources
- The TOY CPU design presentations
- The HACK CPU lectures

# Next week

Verifying the whole system + work week